

T3 - AC -> DC circuit

Integrated Master in Physics Engineering

João Lehodey (96538), Jorge Silva (96545), Pedro Monteiro (93156)

May 8th, 2021

Contents

1	Introduction	1
2	Theoretical Analysis	2
3	Simulation Analysis	2
4	Conclusion	4

1 Introduction

In this laboratory assignment our aim is to design a circuit capable of converting an AC voltage input into a DC voltage output. More specifically, we will convert a voltage input of $230V$ and $50Hz$ into an approximate voltage output of $12V$. To achieve this, we will use diodes, resistors, a transformer and a capacitor.

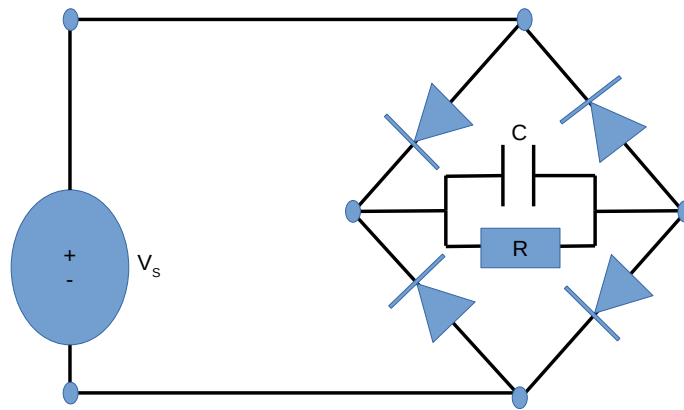


Figure 1: Circuit to be studied

2 Theoretical Analysis

Our Value of n used was 17.03. Therefore we used a voltage source of 13.5 V. We used $R = 20$ Kohm and $C = 20$ F. We reached an outstanding value of merith of 0.09.

Using Octave we reached the following results:

3 Simulation Analysis

Using Ngspice we reached the following results:

Name	Value
ripple	2.620515e-01
average	1.201258e+01

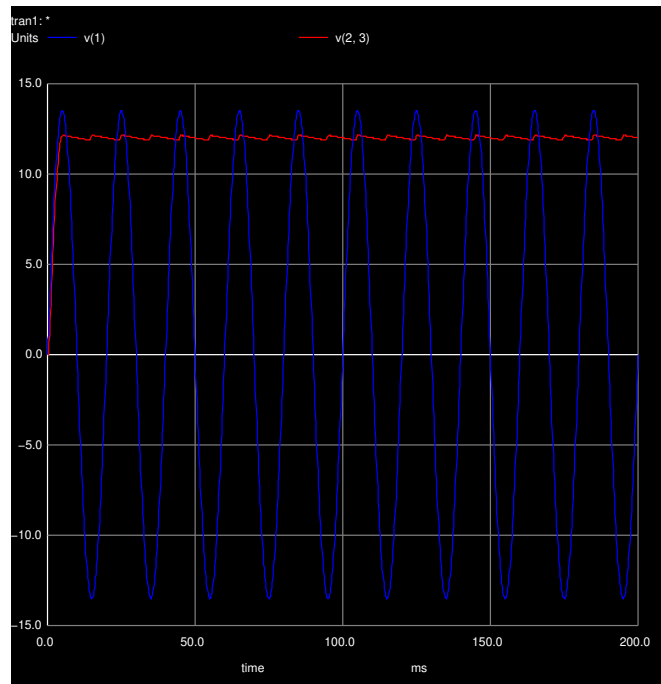


Figure 2: V_o e V_s

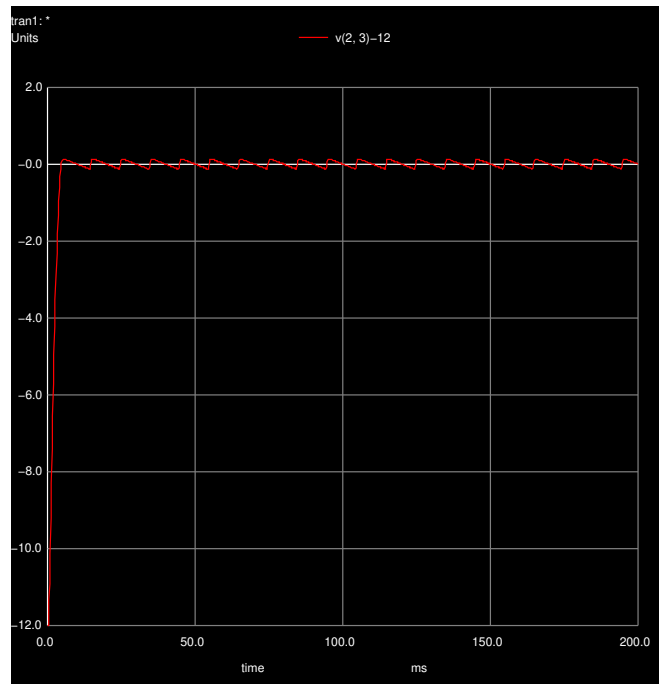


Figure 3: Vo-12

Side by side we reach the following: ...

4 Conclusion